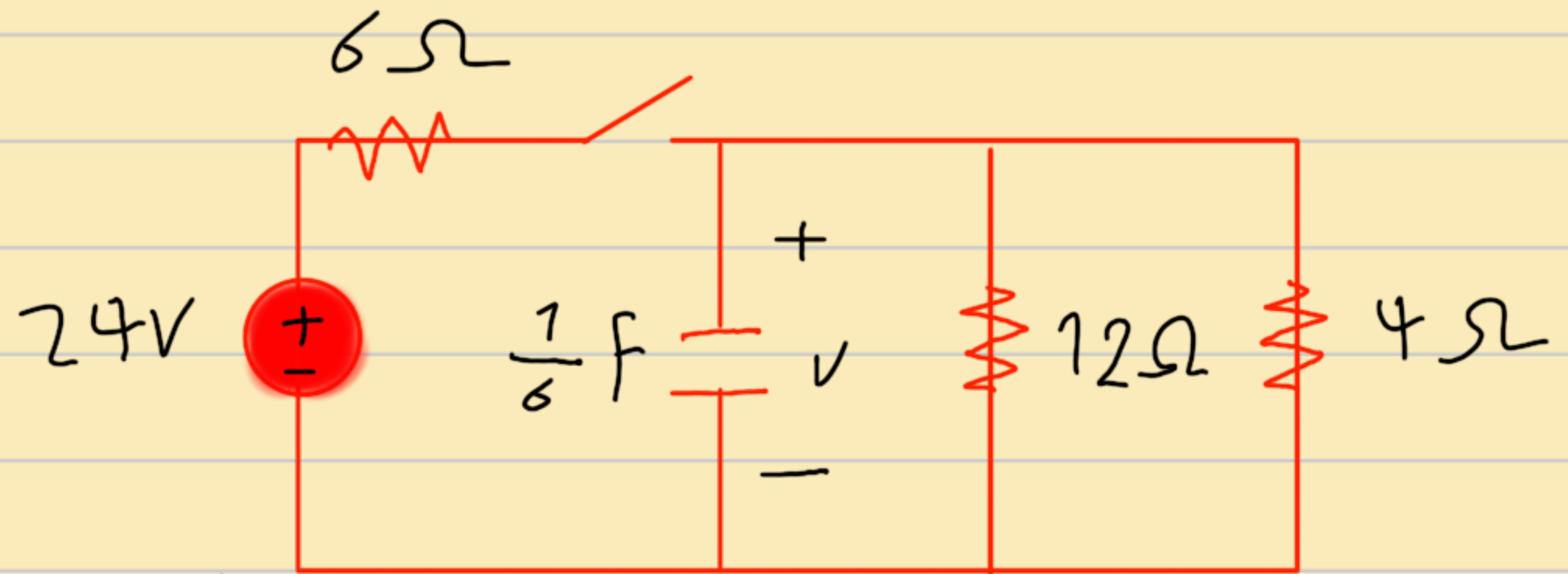


FINAL



RC circuit:-

In the circuit in the figure, the switch has been closed for a long time. It is opened at $t = 0$.



- Find the energy stored in the capacitor at the initial time.
- Find the capacitor voltage at time t .



First :-

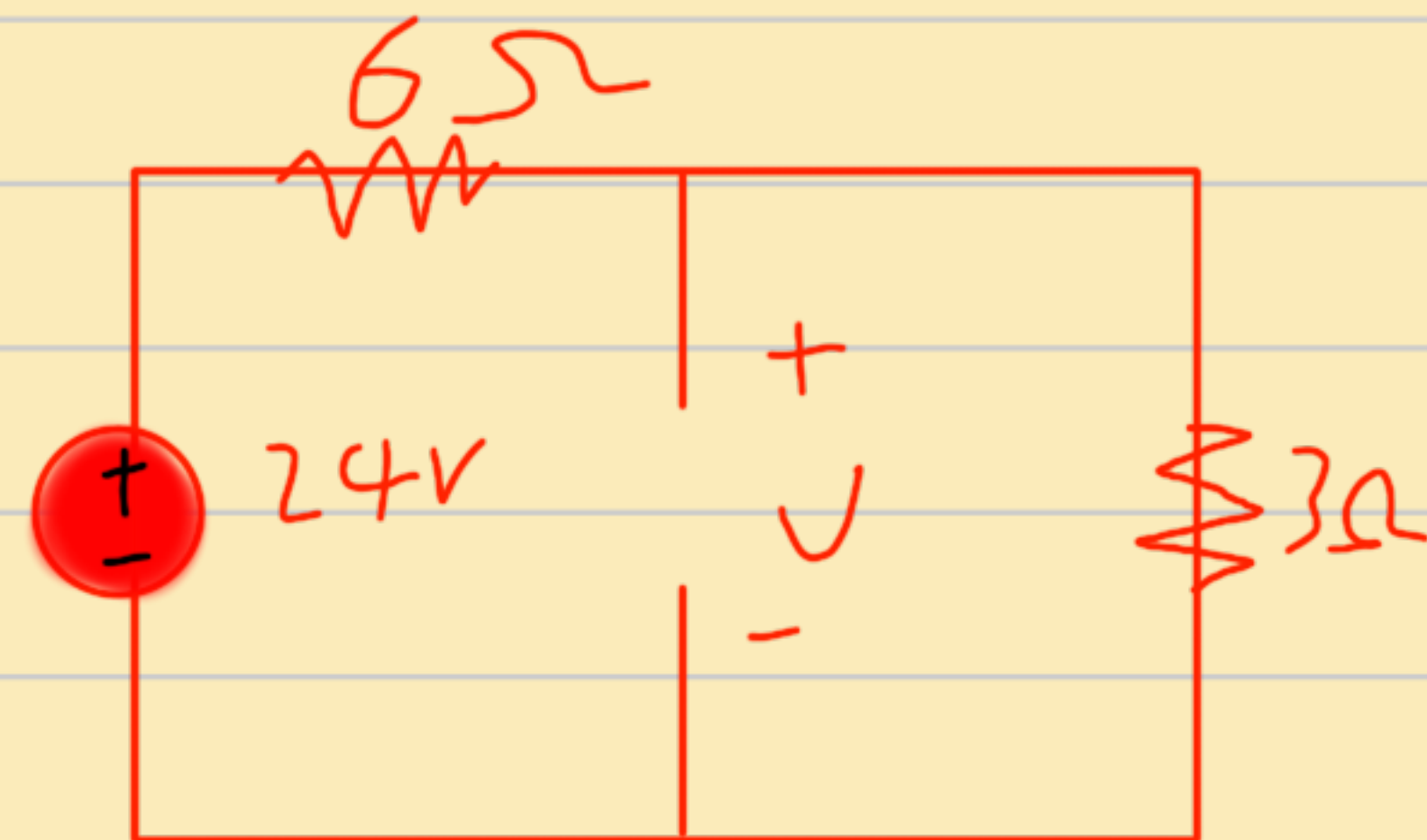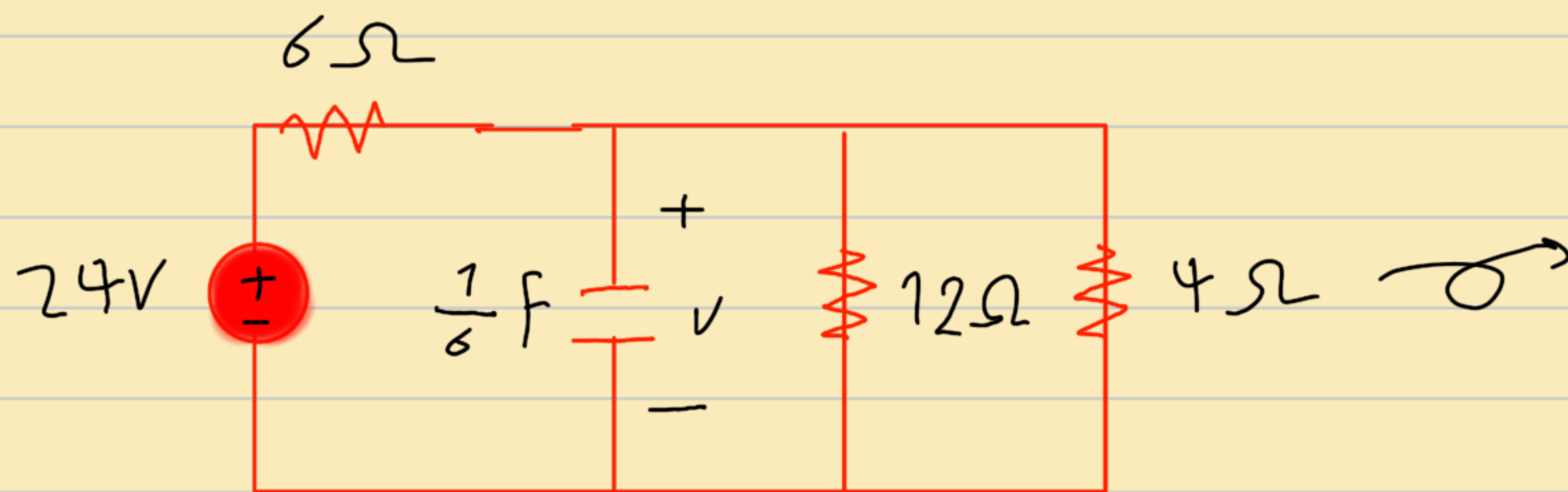

First find V_c :-

$$V_c = \frac{3}{6+3} 24 = 8V \quad V_o = 8V$$

Second :-

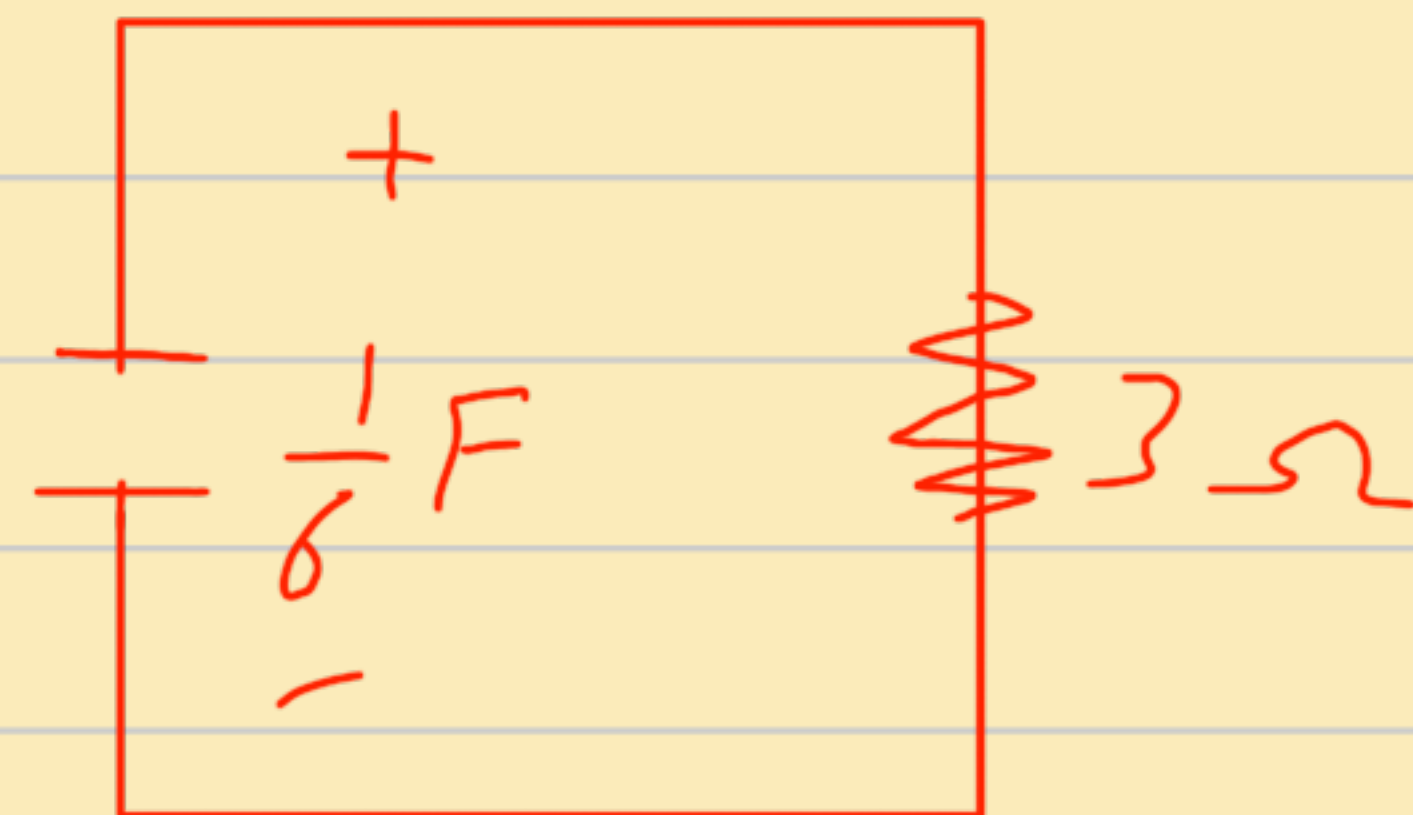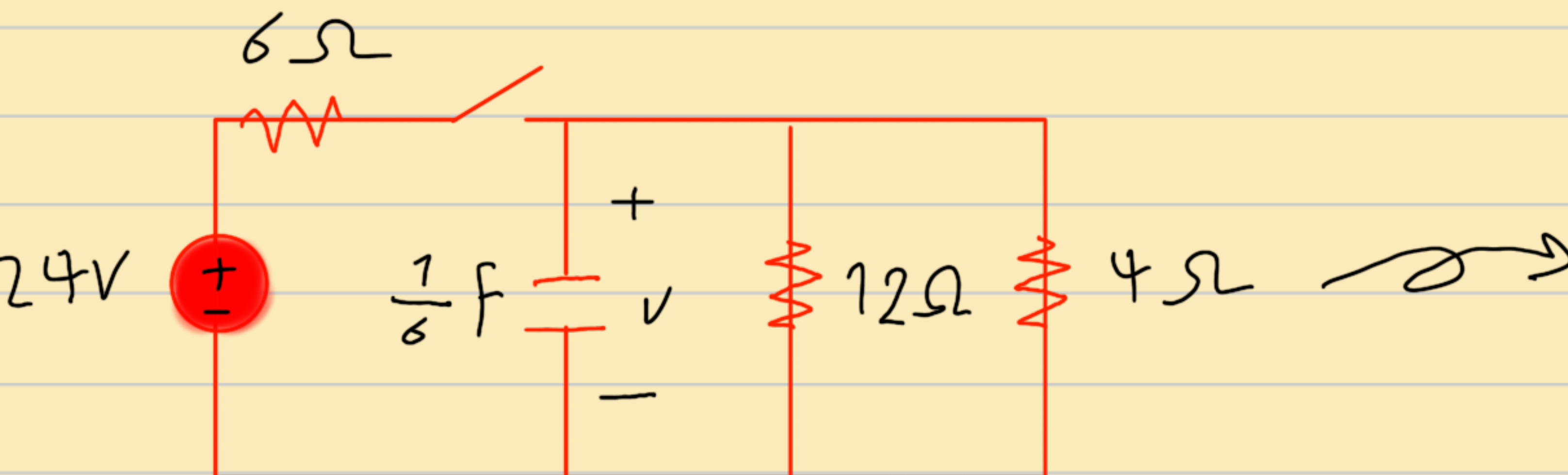

First find τ :-



$$T = RC = 3 \times \frac{1}{6} = 0.5s$$

second find $V_c(t)$:-



$$V_c(t) = V_0 e^{-t/RC} = 8 e^{-t/0.5} = 8 e^{-2t} V$$

RL circuit:-

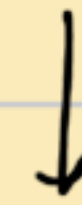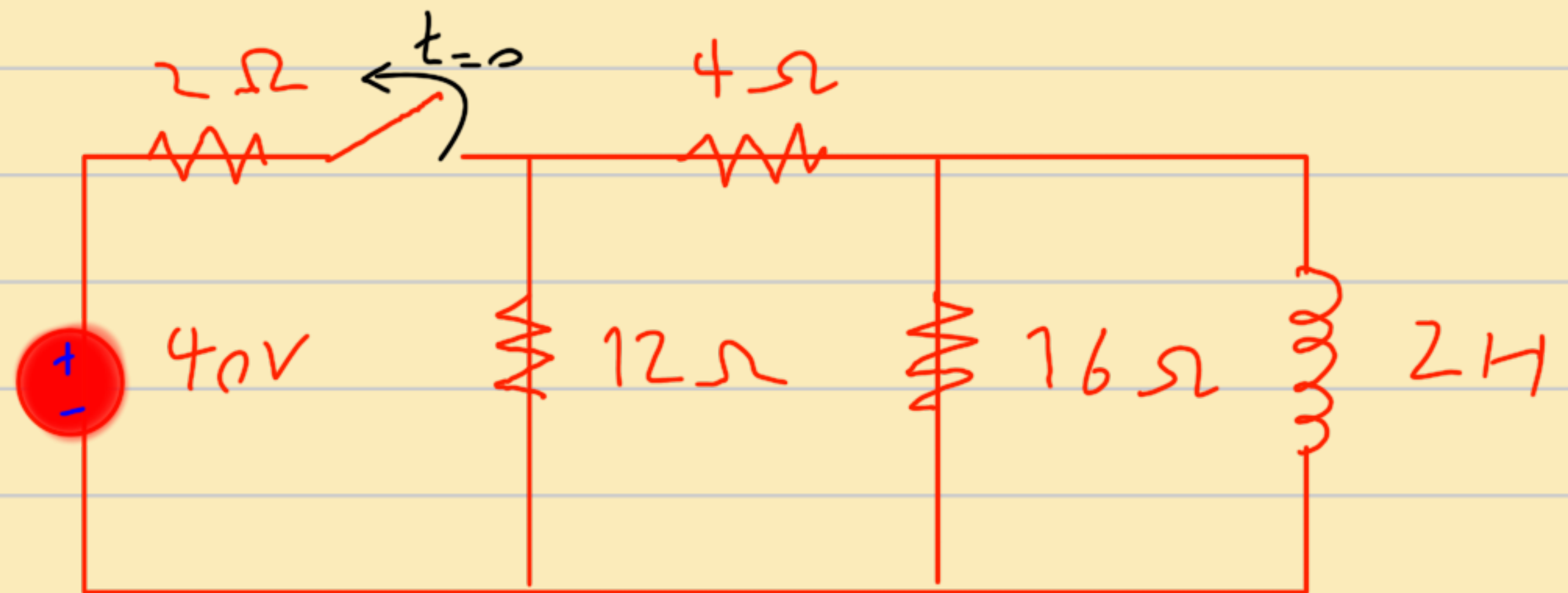The switch remains closed for a sufficient time. At time $t=0$ the switch opens. Calculate i_t for $t > 0$.



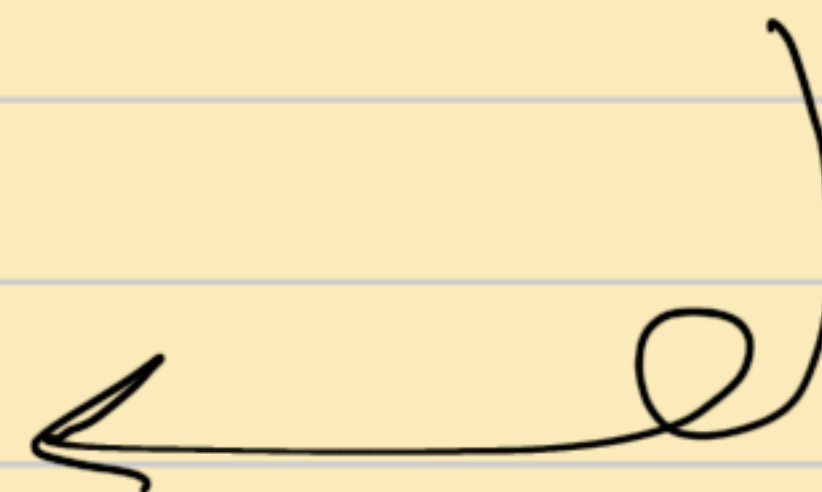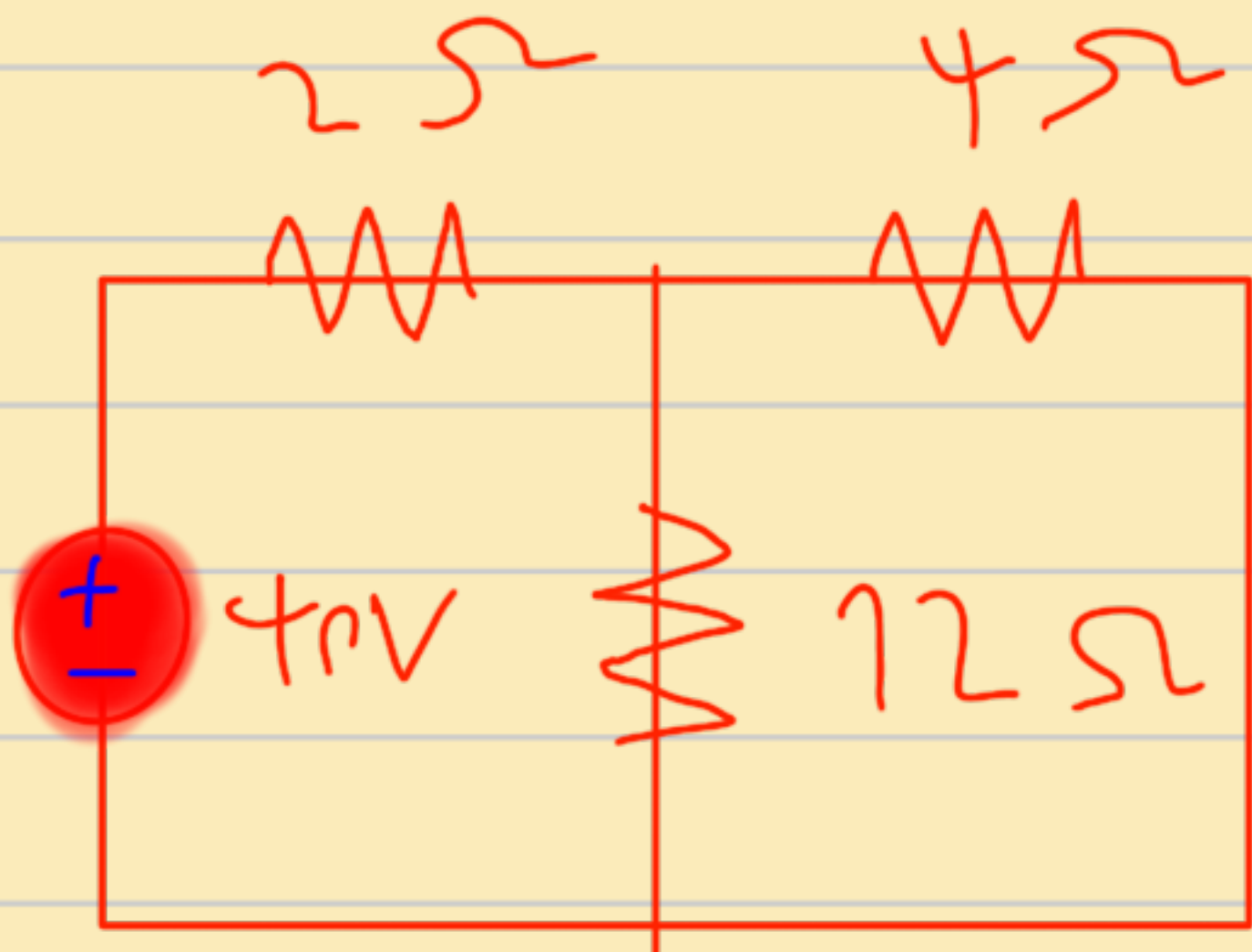
When the switch is closed the coil will act as a short circuit. therefore the 16Ω resistor will be short circuited.



first step Find R_{eq} :-

$$R_{eq} = \frac{2 \times 12}{2 + 12} = 1.71 \Omega$$

$$1.71 + 4 = 5.71 \Omega$$

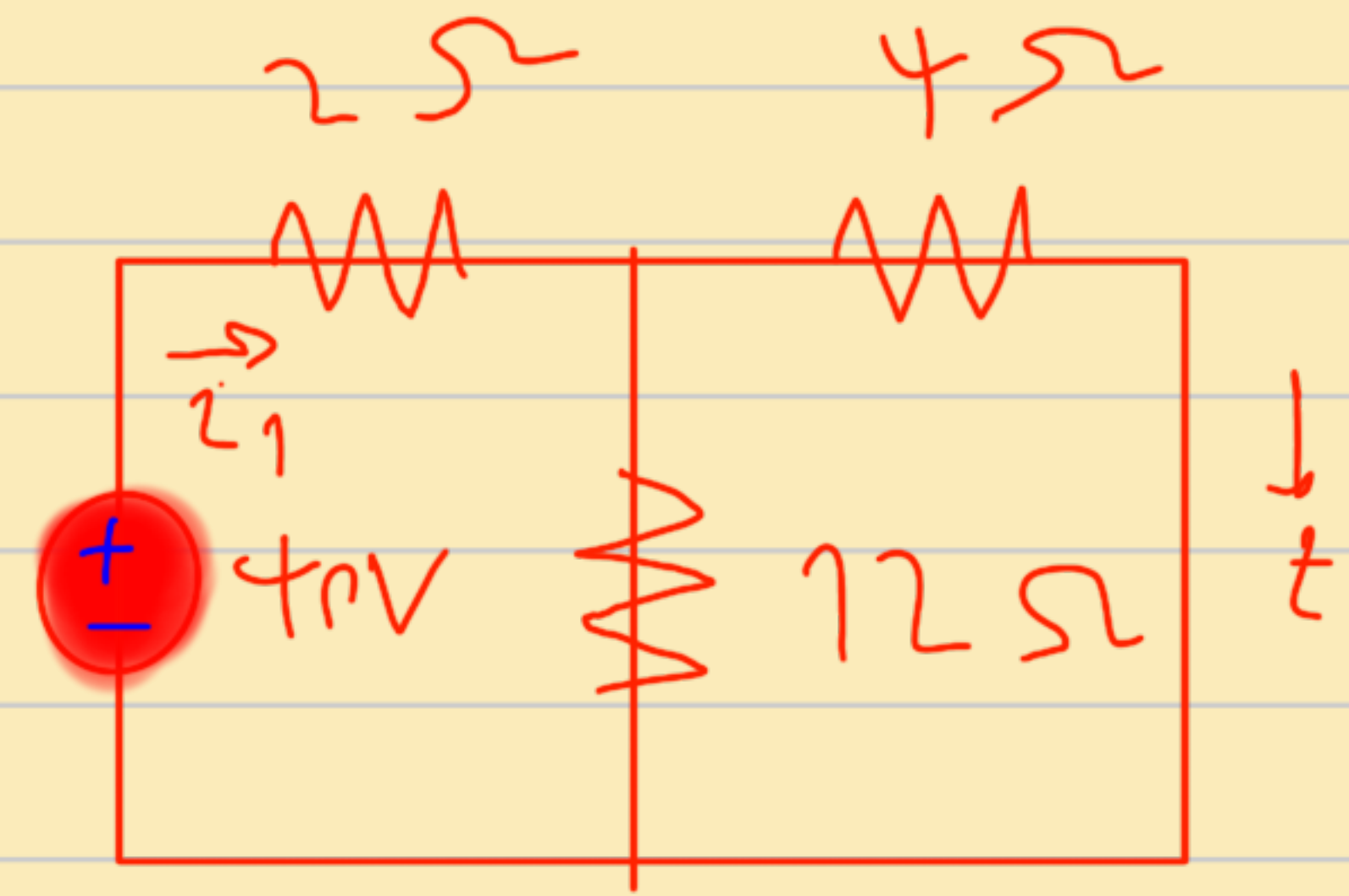

second step find i_1 which flowing in R_{eq} :-

$$i_1 = \frac{V}{R_{eq}} = \frac{4}{5.71} = 7.005 A$$

third step find $i(t)$:-

• From the current Divider circuit Rule.


! $i(t)$ which is flowing in short circuit !

$$i(t) = \frac{12}{12 + 4} \cdot 7.005 = 5.25 A$$

- Since the current in the inductor cannot change instantly;

$$i(0) = i(0^-) = 5.25 \text{ A}$$

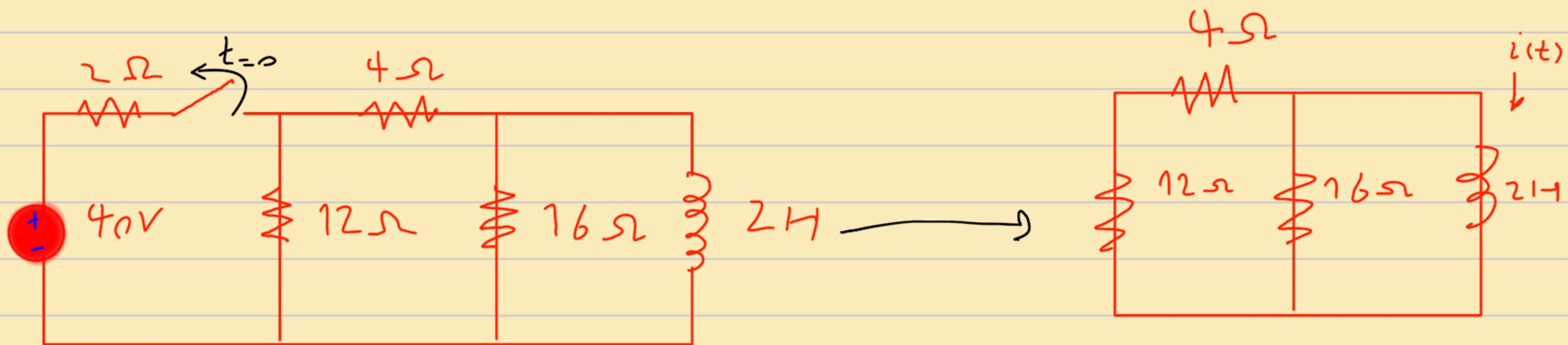After the switch is opened the voltage source will be deactivated.



First step find R_{eq} :-

$$R_{eq} = 12 + 4 = 16$$

$$\frac{16 \times 16}{16 + 16} = 8 \Omega$$

second step Find τ :-

$$\tau = \frac{L}{R_{eq}} = \frac{2}{8} = 0.25s$$


Last step Find $i(t)$:-

$$i(t) = i_0 e^{-t/\tau}$$

$$i(t) = 5.25 e^{-t/0.25}$$

$$A = 5.25 e^{-4t} A$$

0 Part

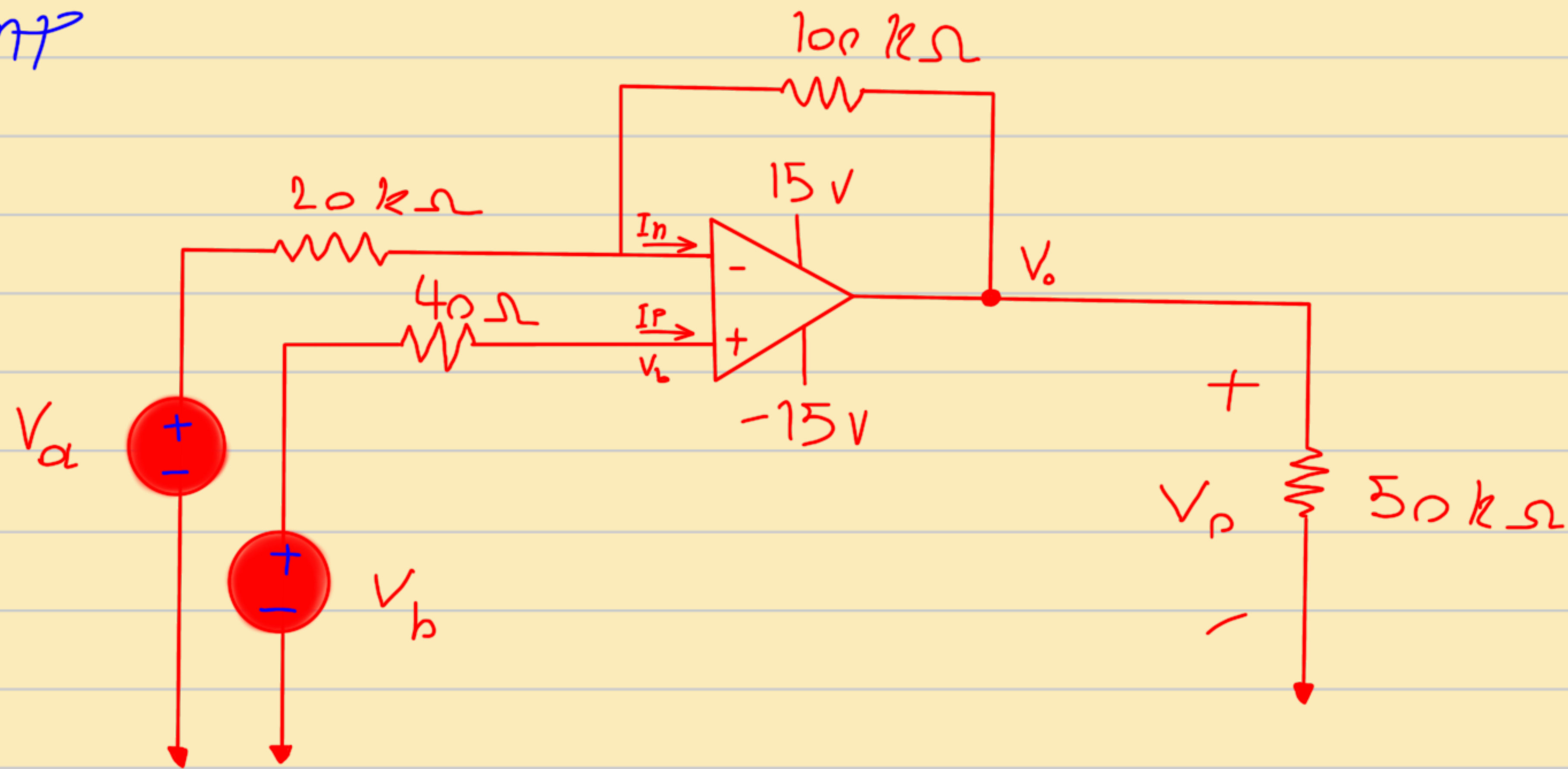

a) Given that $V_a = 4V$, $V_b = 0V$ then find V_o

b) Given that $V_a = 2V$, $V_b = 0V$ then find V_o

c) Given that $V_a = 2V$, $V_b = 1V$ then find V_o

d) Given that $V_a = 1V$, $V_b = 2V$ then find V_o

first find the equation:-

$$\frac{V_n - V_a}{20} + \frac{V_n - V_o}{100} = 0$$

$$I_n = I_p = 0 \longrightarrow V_n = V_p = V_b$$

$$\frac{V_b - V_a}{20} + \frac{V_b - V_o}{100} = 0$$

$$5V_b - 5V_a + 1V_b = V_o$$

$$6V_b - 5V_a = V_o$$

a) $V_a = 4V$ $V_b = 0V$

$$6(0) - 5(4) = -20 \longrightarrow a = -20$$

b) $V_a = 2V$ $V_b = 0V$

$$6(0) - 5(2) = -10 \longrightarrow b = -10$$

c) $V_a = 2V$ $V_b = 1V$

$$6(1) - 5(2) = -4 \longrightarrow c = -4$$

d) $V_a = 1V$ $V_b = 2V$

$$6(2) - 5(1) = 7$$

$$\longrightarrow d = 7$$